
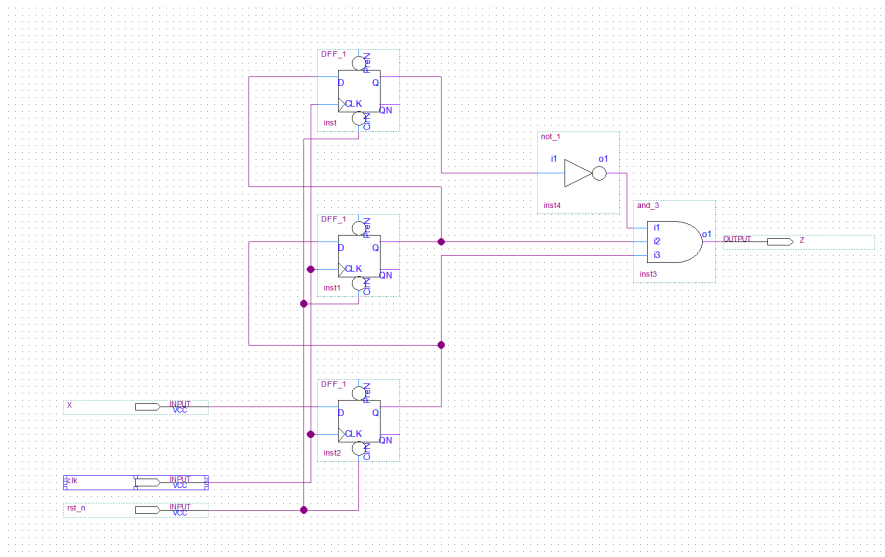


1. Sequence Detector:

SD:

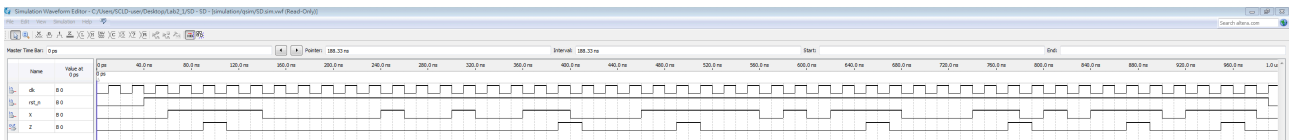


SD waveform:




2. Accumulator:


FA1:

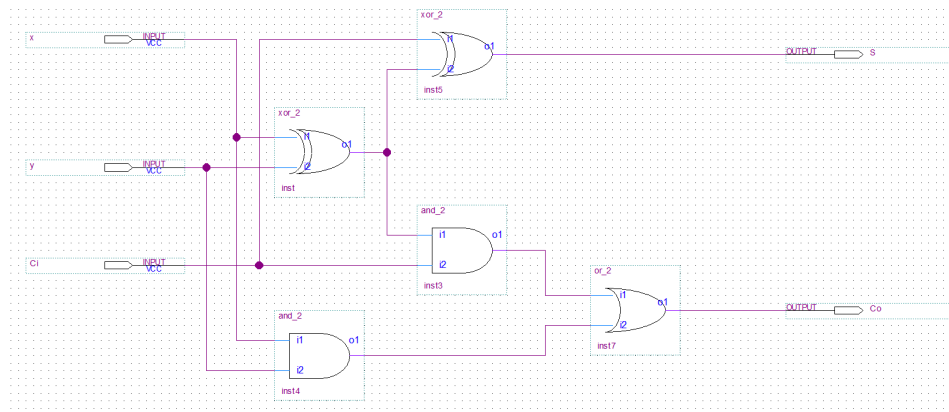


FA4:

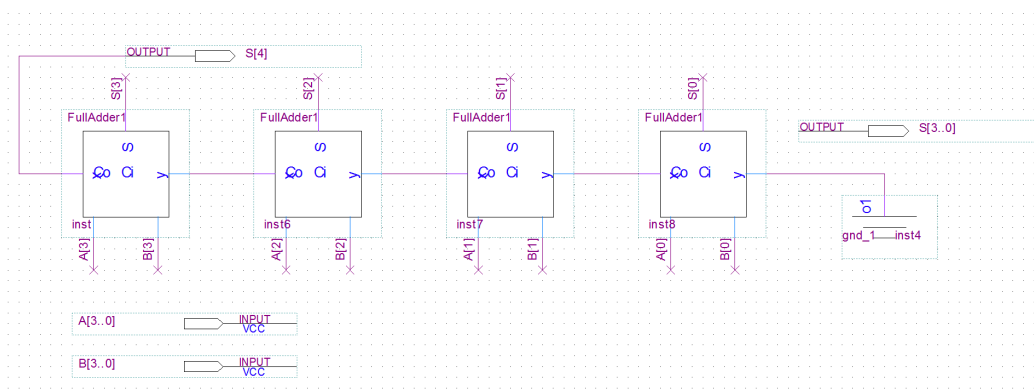


MUX4:

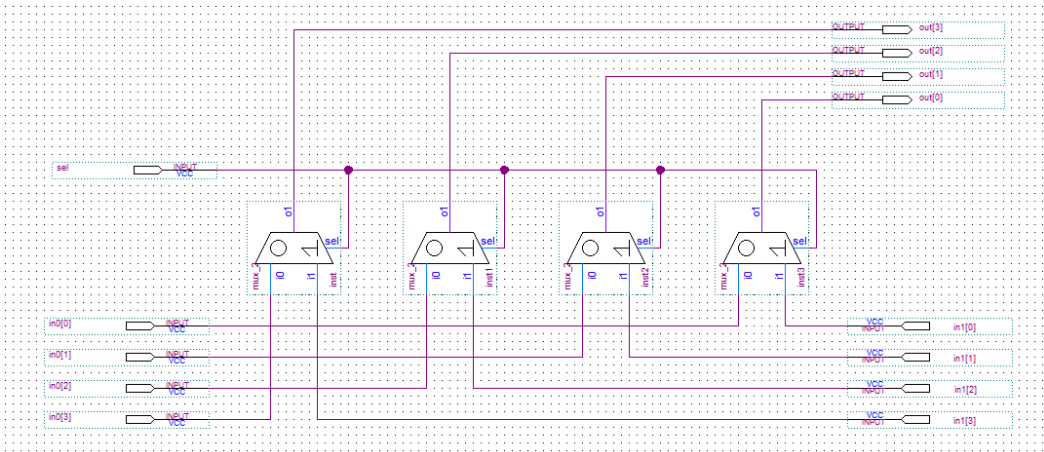


DataReg:

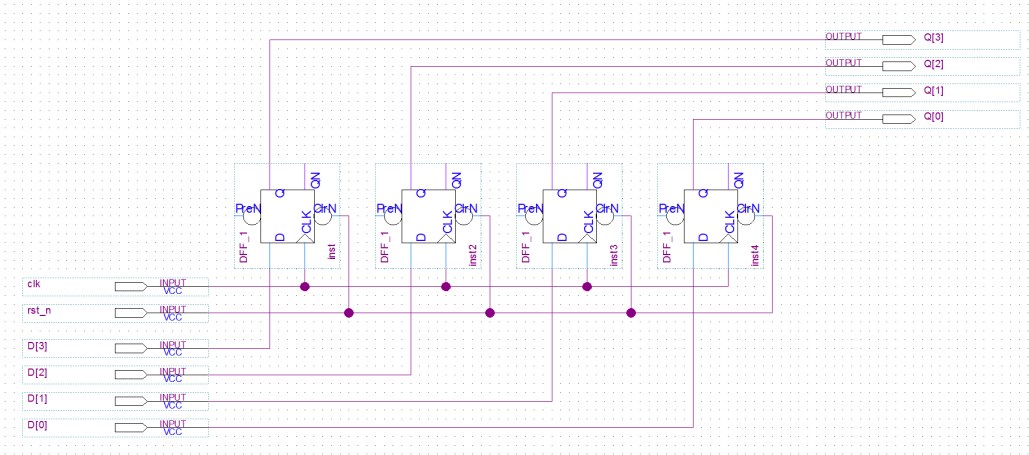


Controller(AC4):

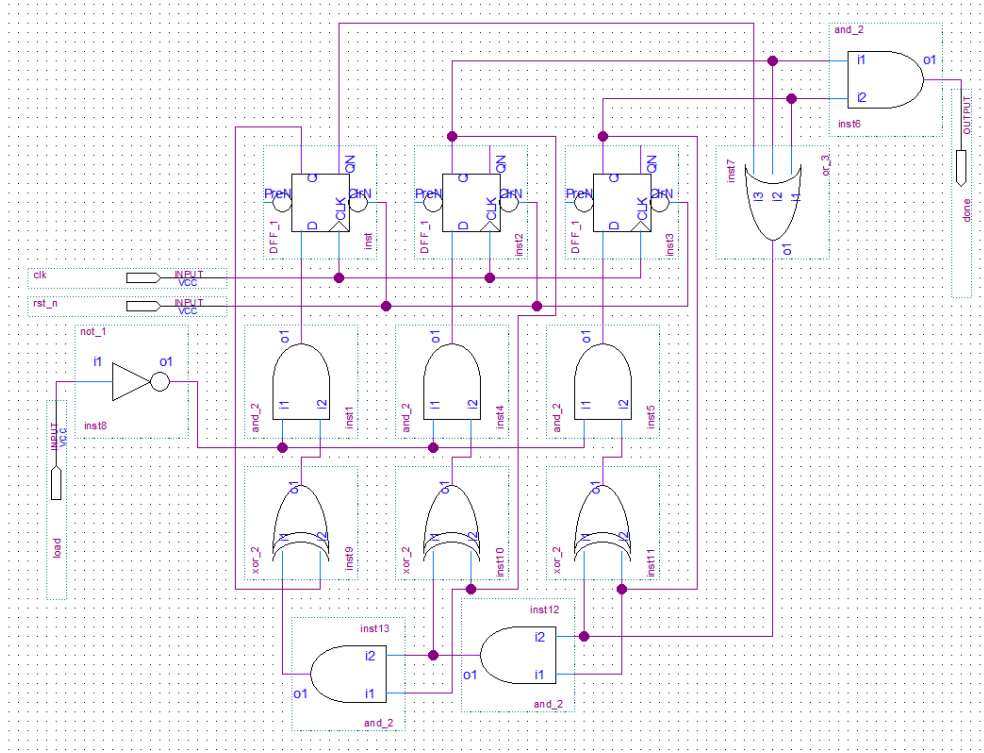

AC4:

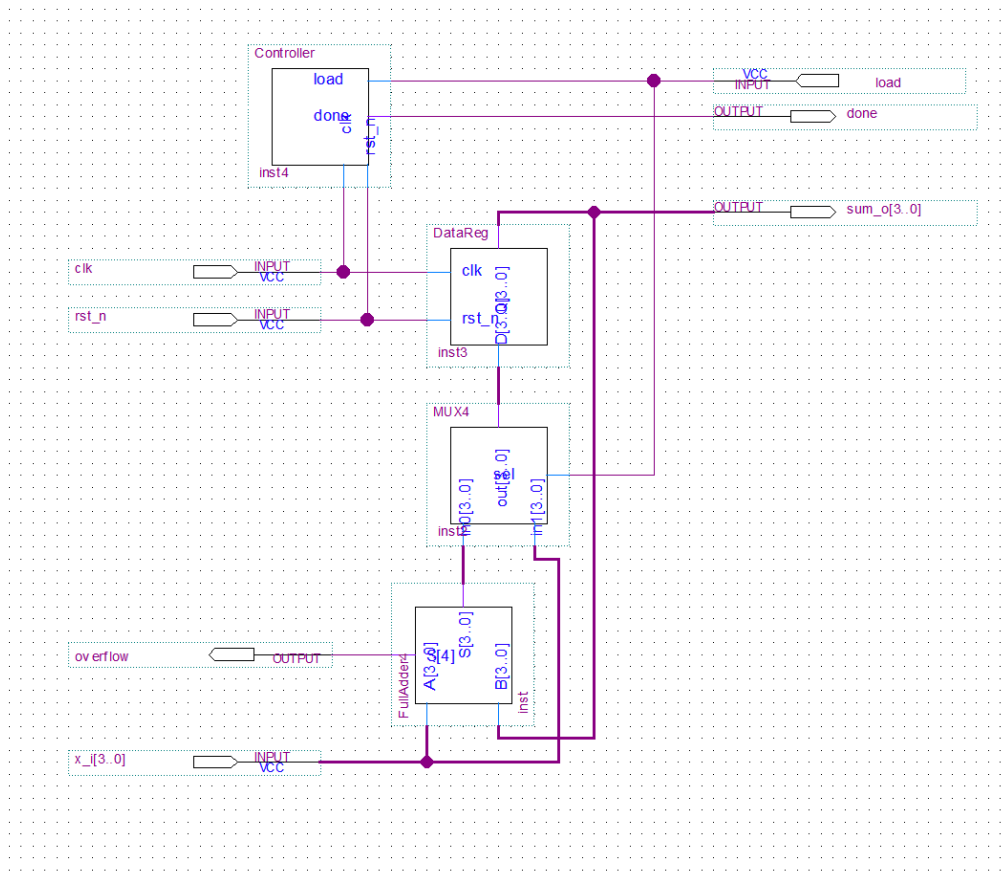


AC4 waveform:

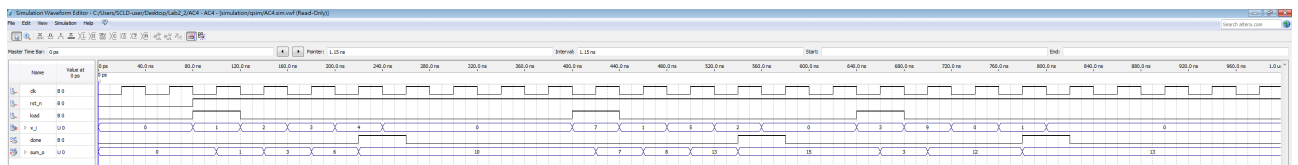


3. Divider:


FS1:

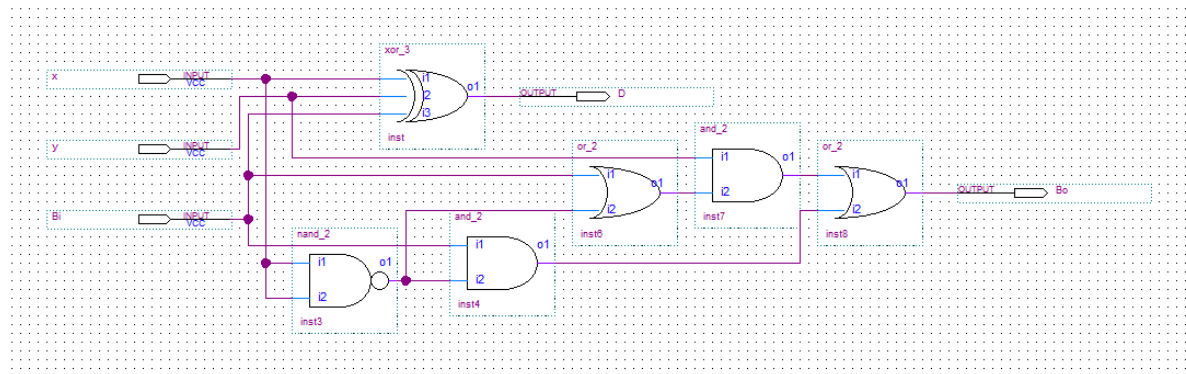


FS4:

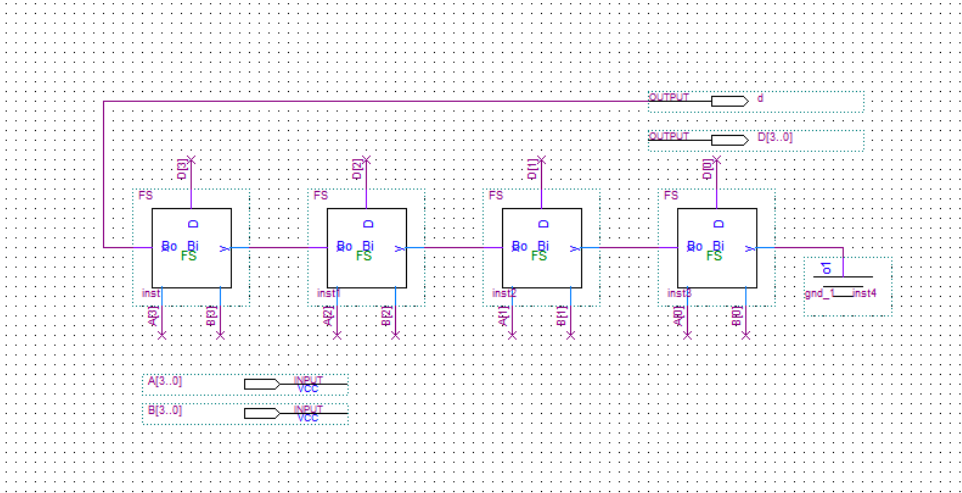


MUX4:

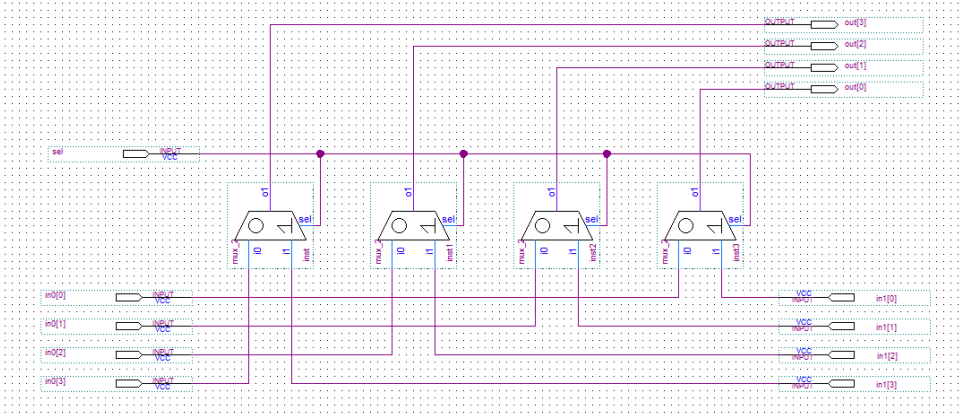


DataReg:

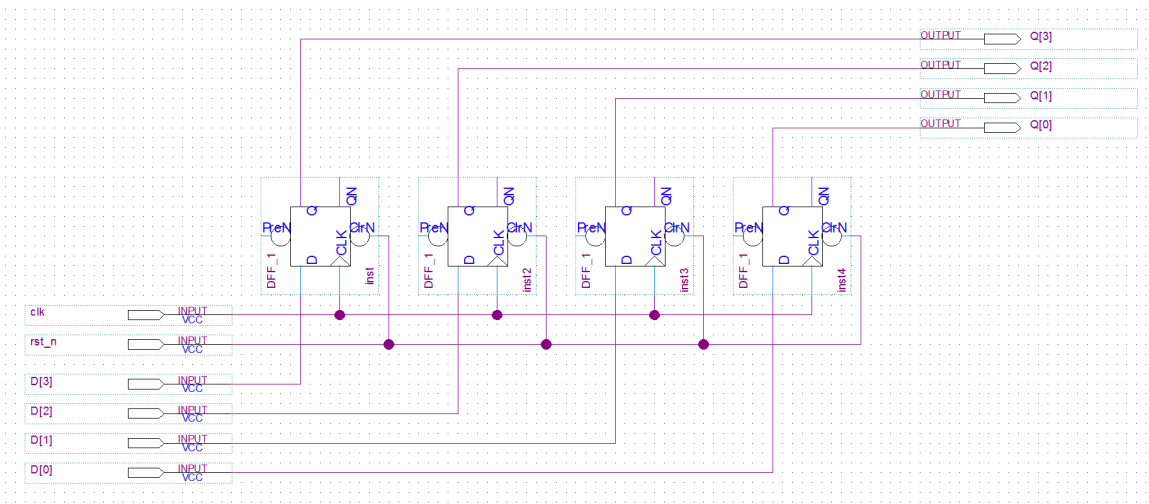


Controller(DV4):

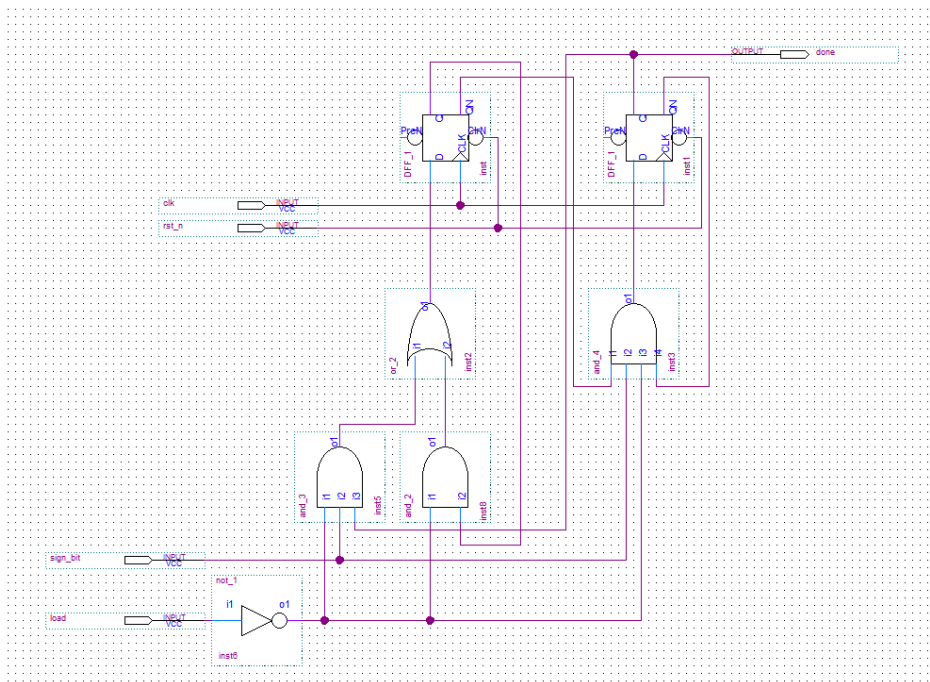

Counter:

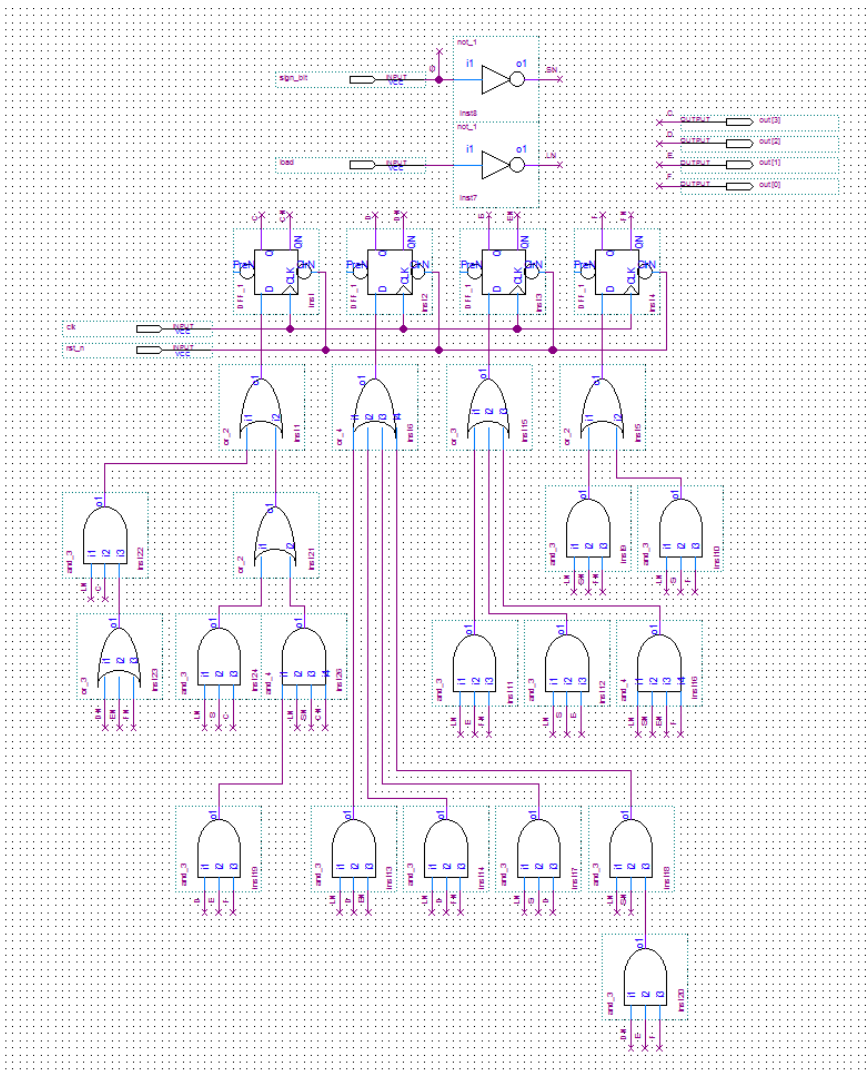

DV4:

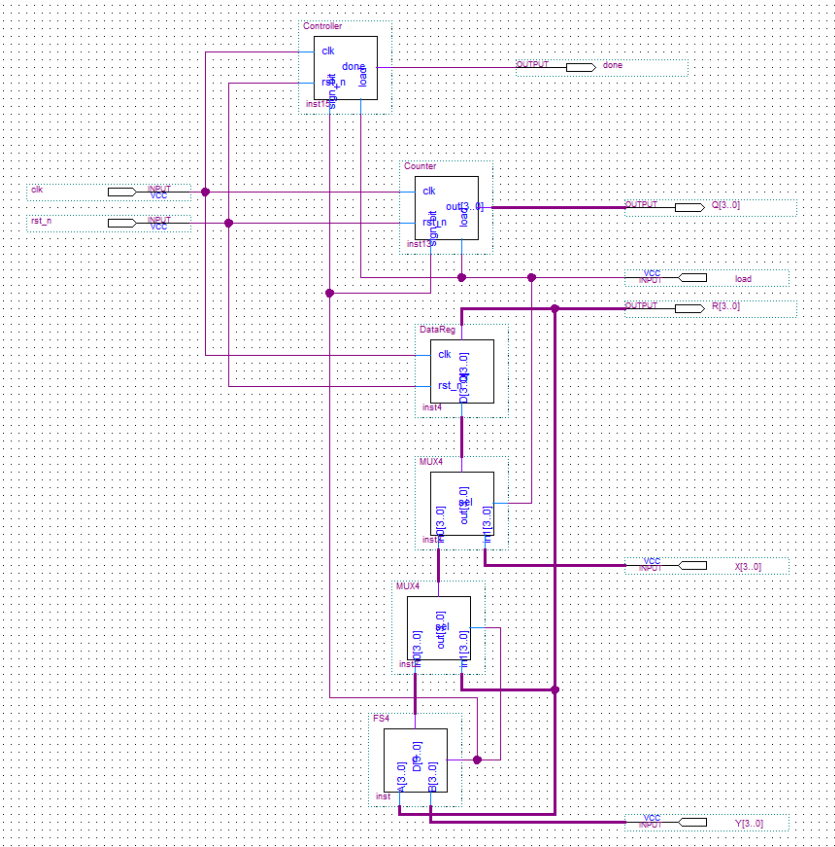

DV4 waveform:

